GFSK CH00	GFSK CH39
Reference	Reference
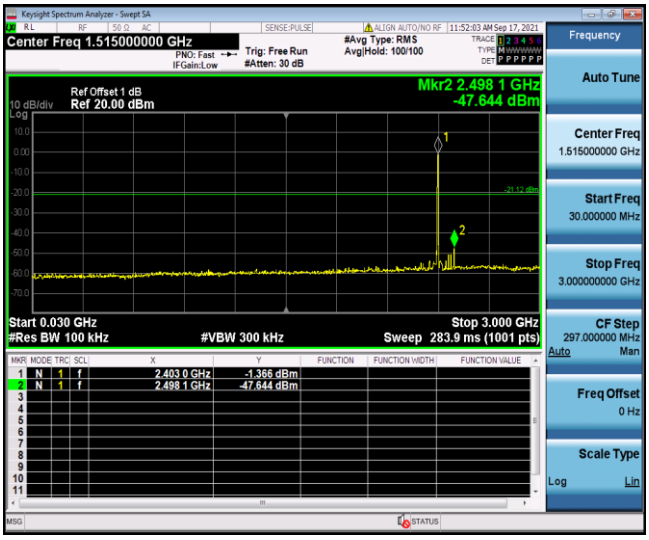	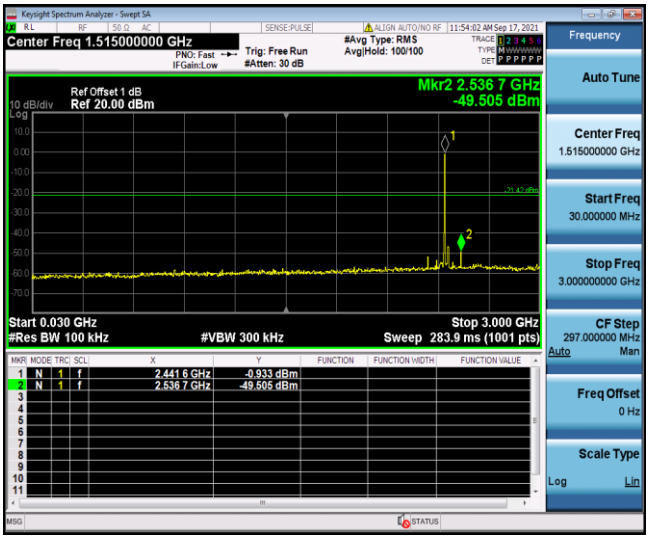
30MHz-3GHz	30MHz-3GHz
3GHz-25GHz	3GHz-25GHz

GFSK CH78	π/4DQPSK CH00
	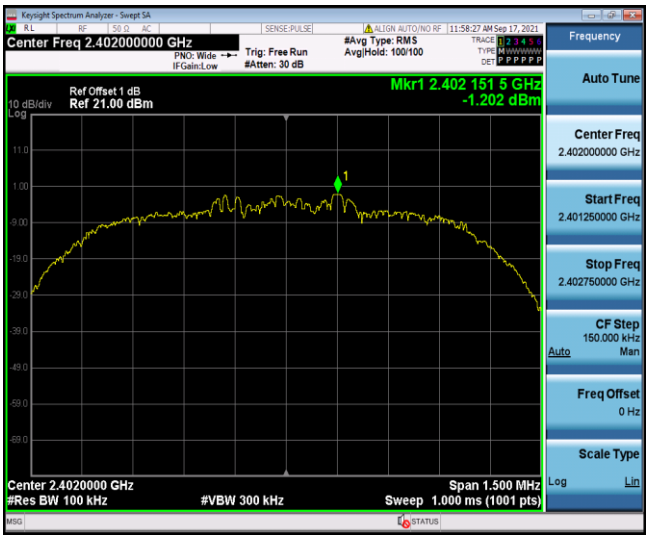
Reference	Reference
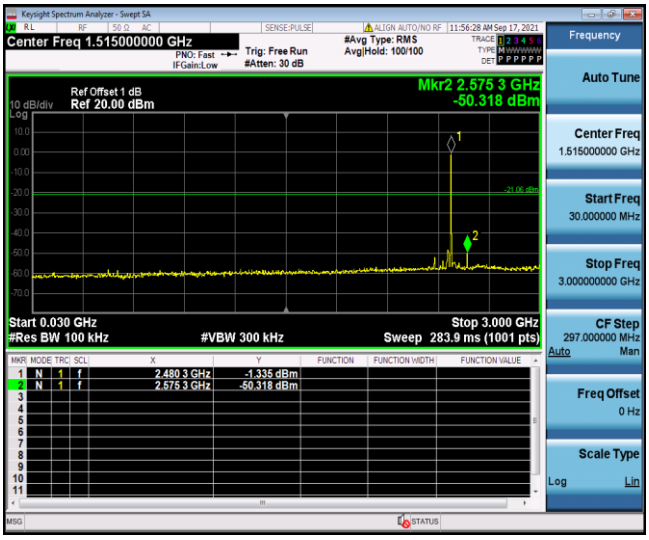	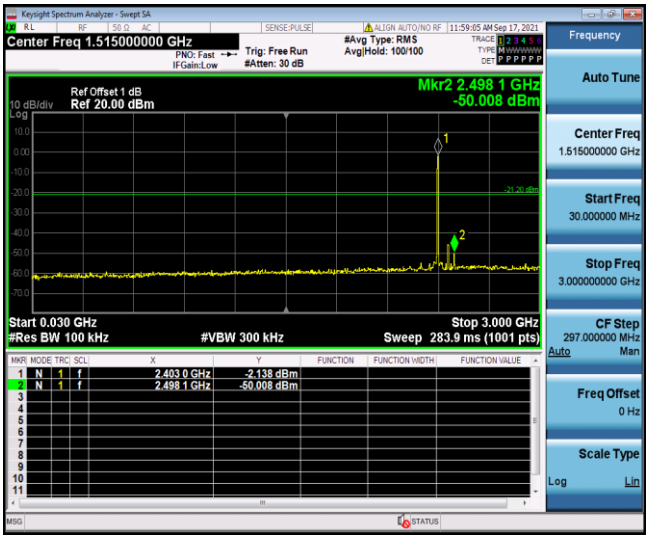
30MHz-3GHz	30MHz-3GHz
	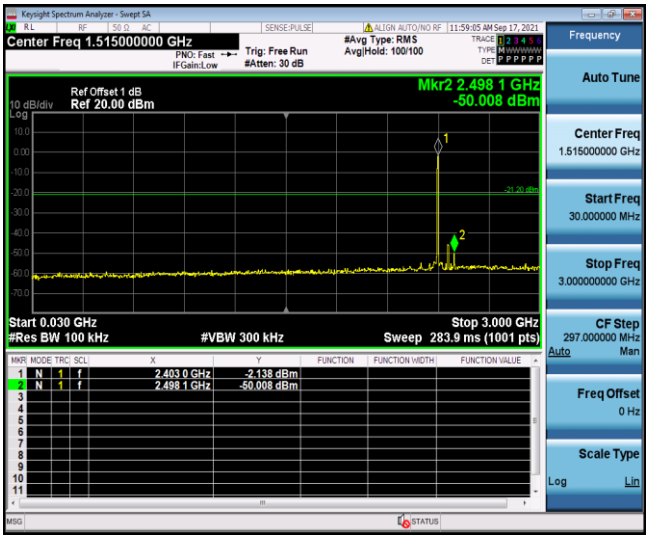
3GHz-25GHz	3GHz-25GHz

π/4DQPSK CH39	π/4DQPSK CH78
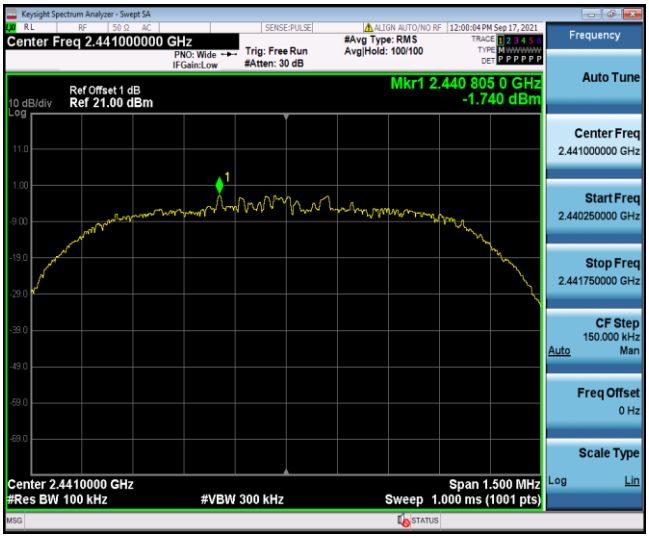	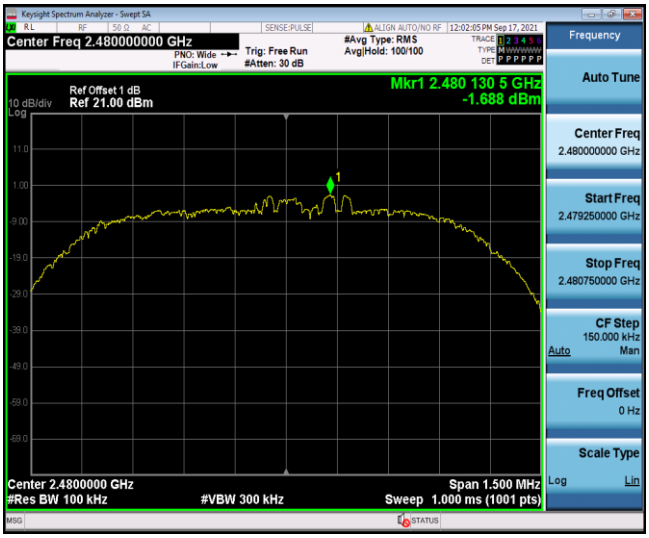
Reference	Reference
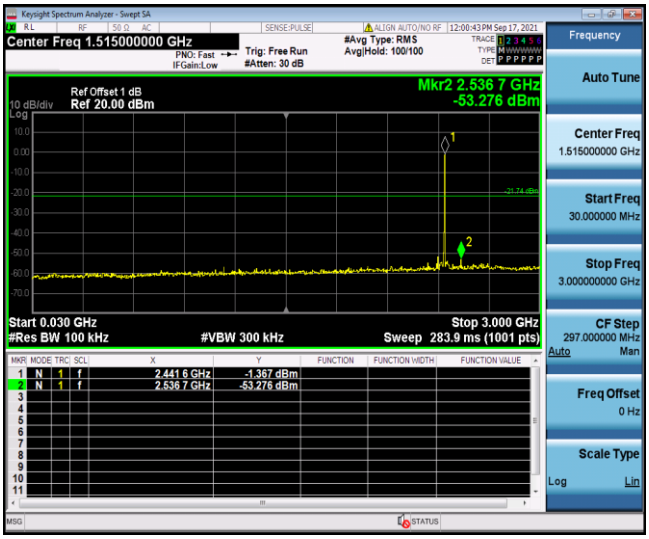	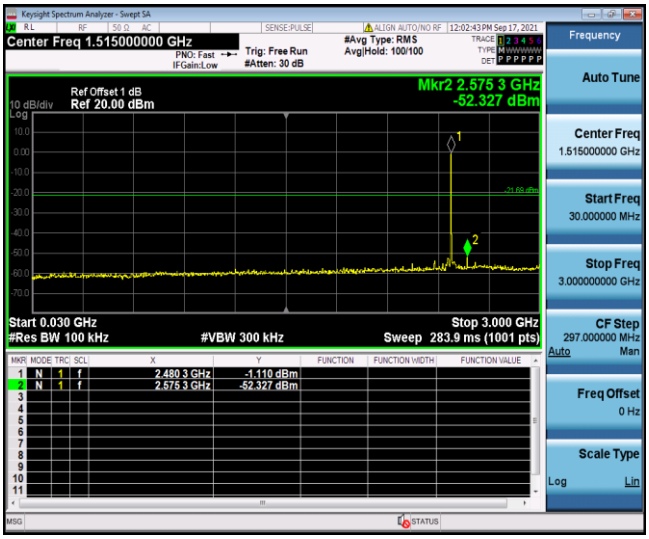
30MHz-3GHz	30MHz-3GHz
3GHz-25GHz	3GHz-25GHz

8DPSK CH00	8DPSK CH39
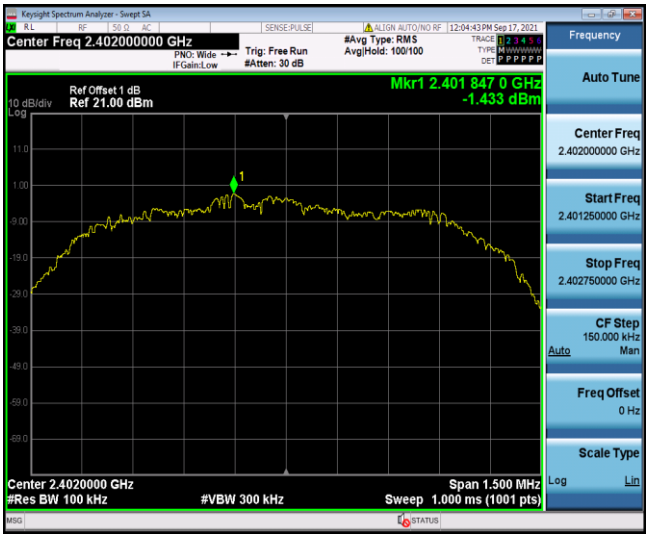	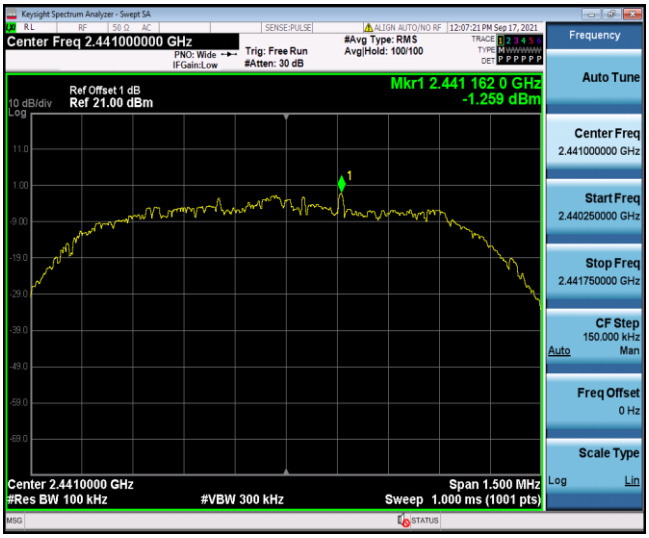
Reference	Reference
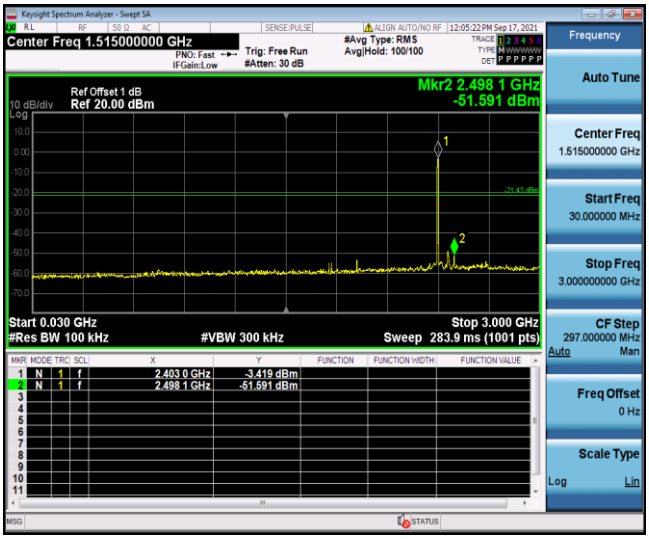	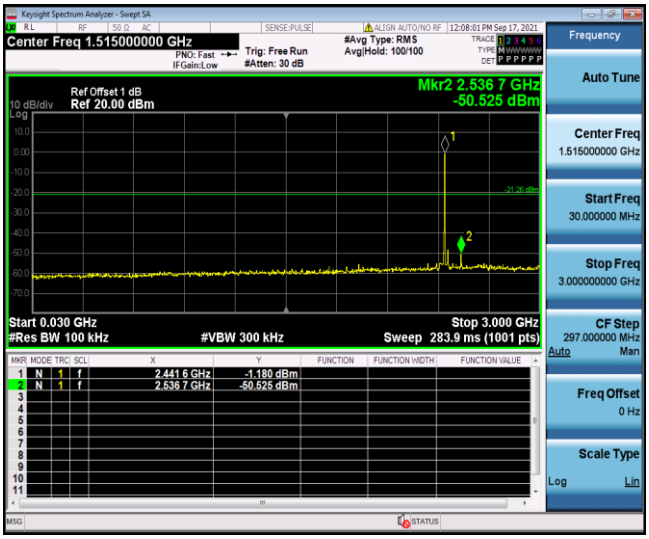
30MHz-3GHz	30MHz-3GHz
3GHz-25GHz	3GHz-25GHz

8DPSK CH78

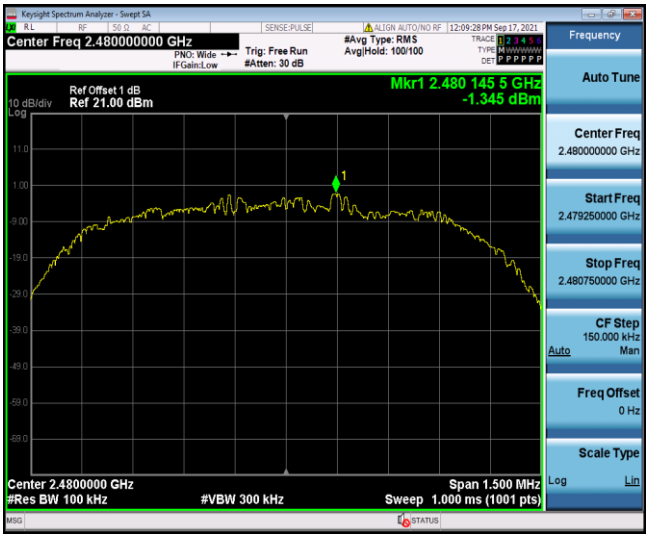

Reference

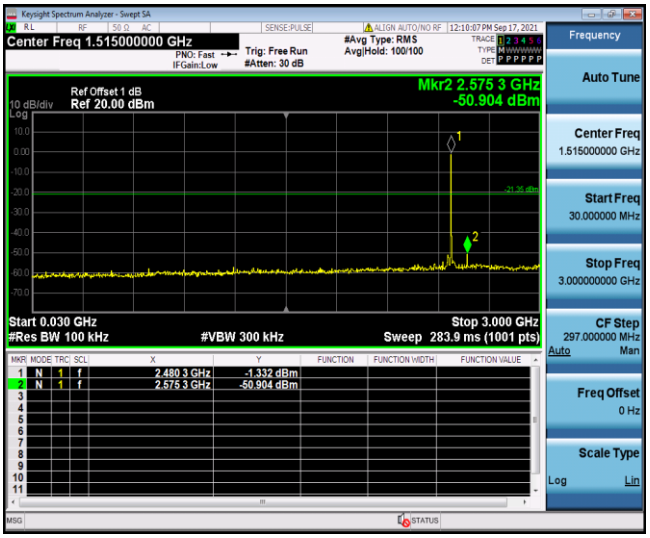

30MHz-3GHz

3GHz-25GHz

Band-edge Measurements for RF Conducted Emissions:

GFSK

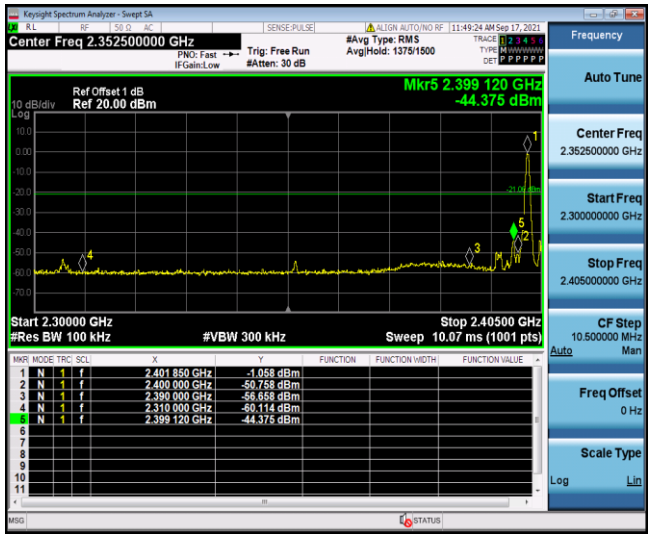

Left Band edge hoping off

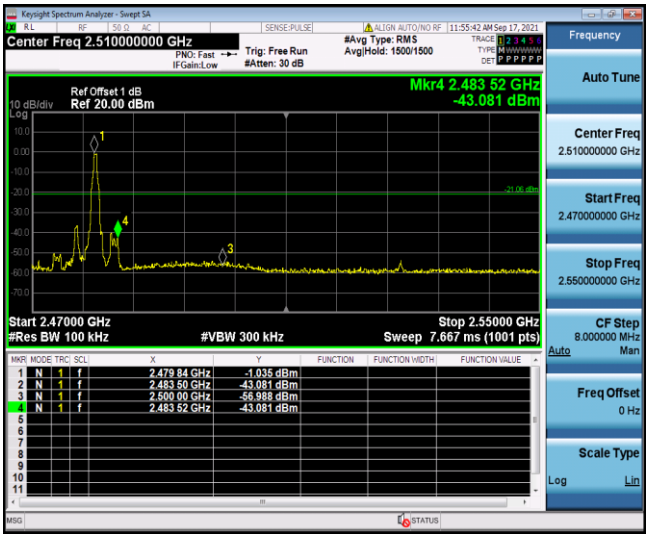

RightBand edge hoping off

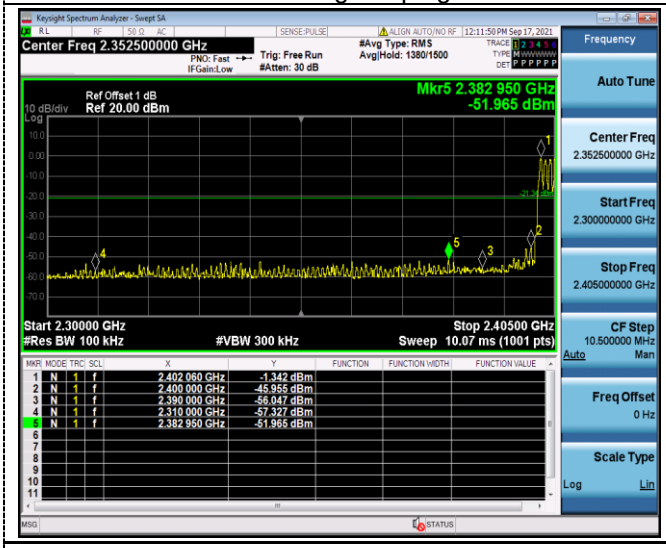

Left Band edge hoping on

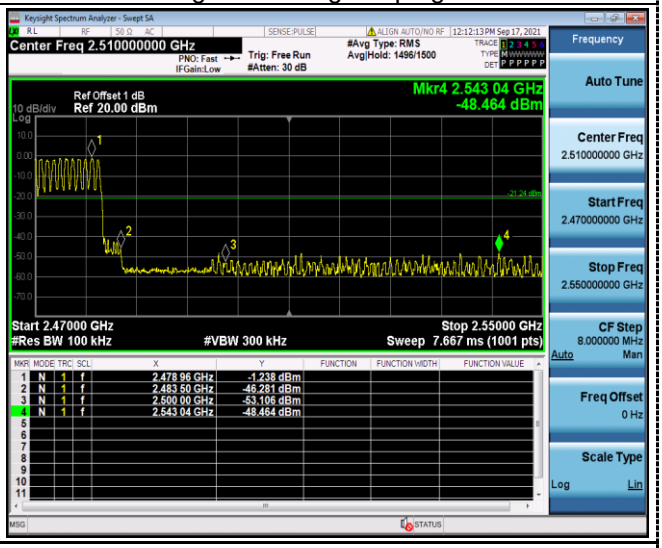

RightBand edge hoping on

π/4DQPSK

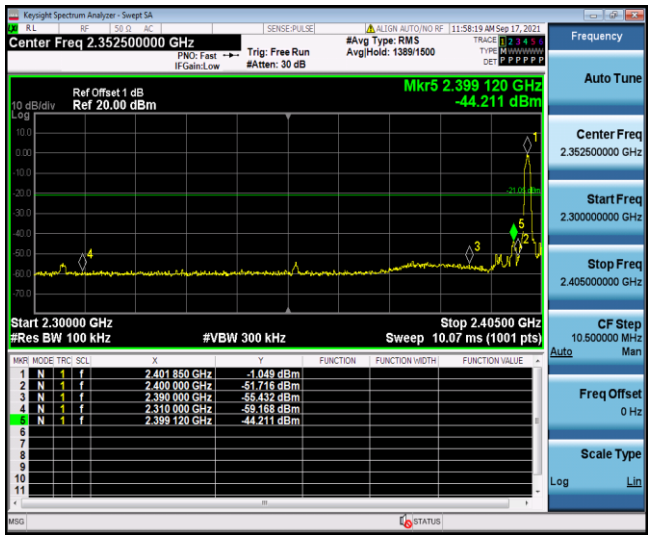

Left Band edge hoping off

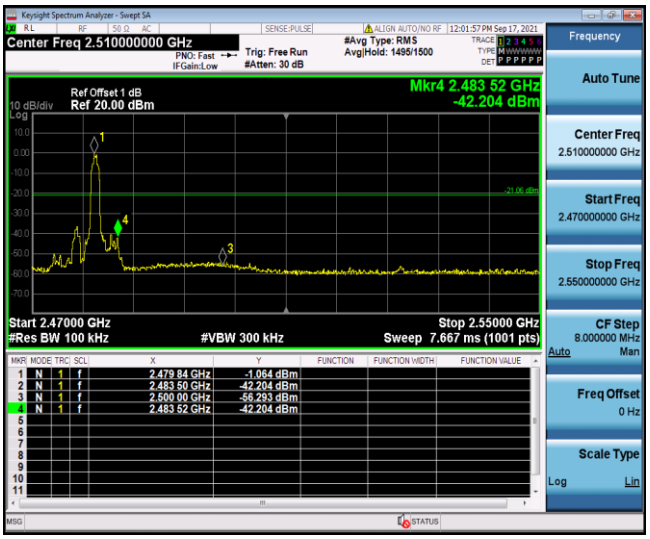

RightBand edge hoping off

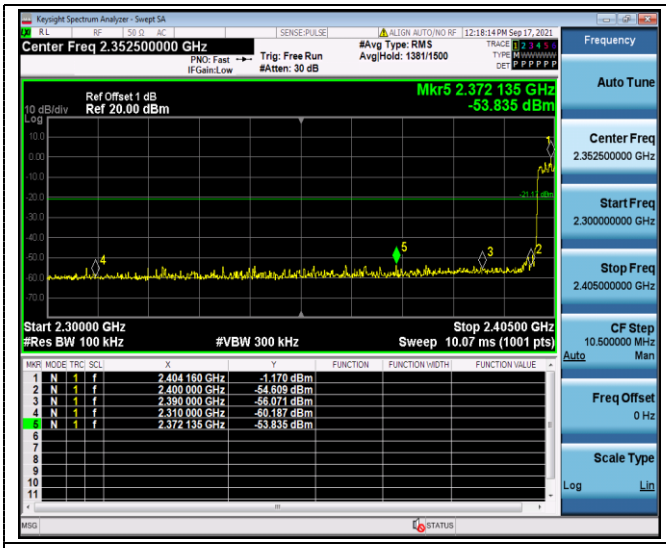

Left Band edge hoping on

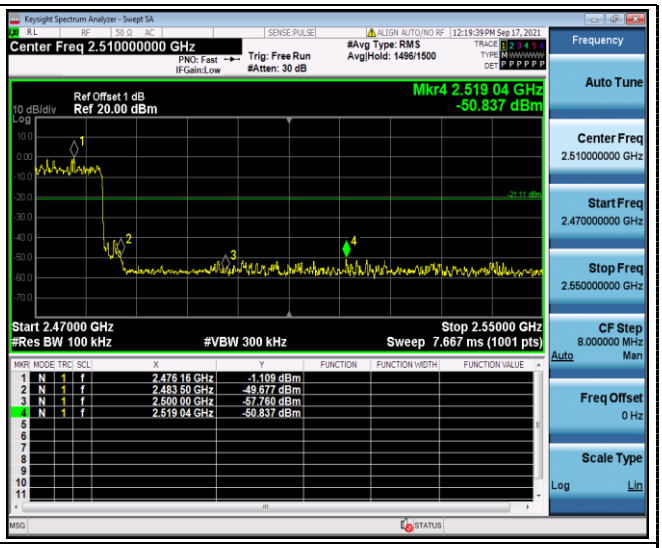

RightBand edge hoping on

8DPSK

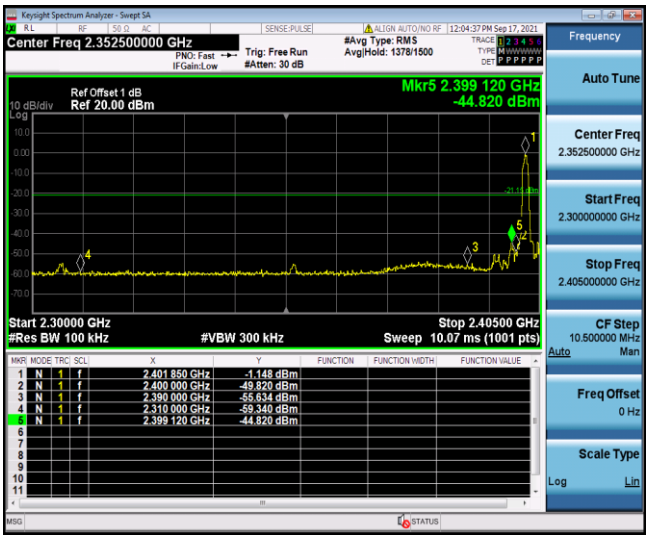

Left Band edge hoping off

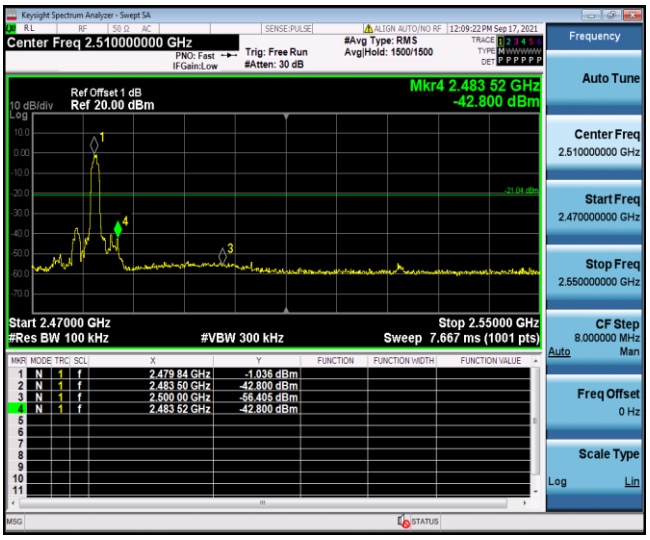

RightBand edge hoping off

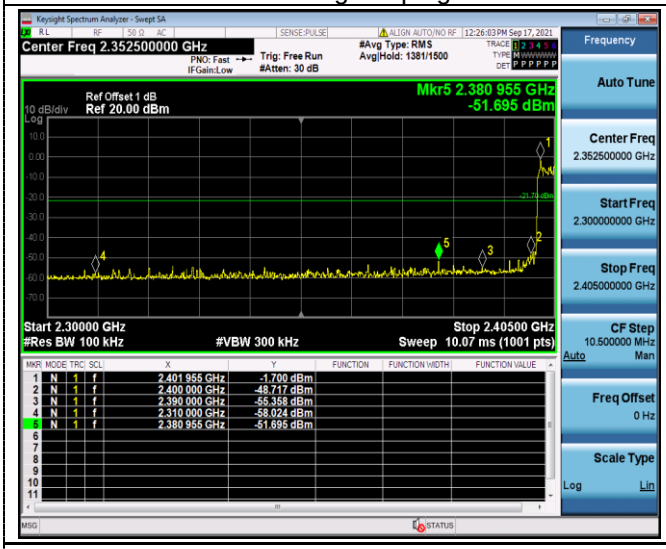

Left Band edge hoping on

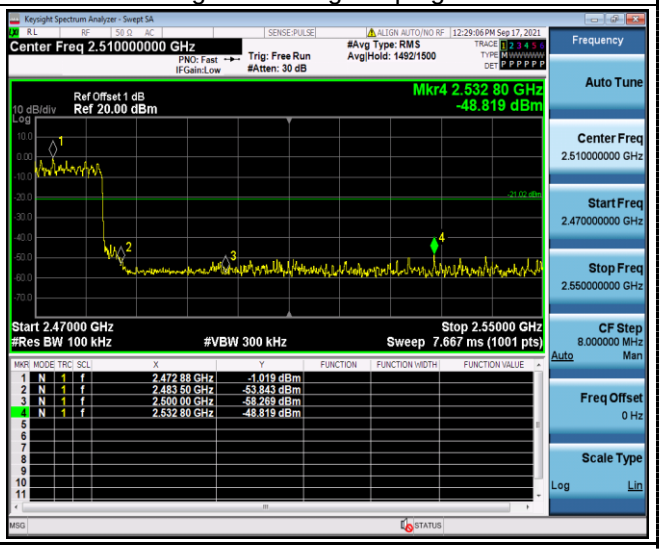

RightBand edge hoping on

4.9 Pseudorandom Frequency Hopping Sequence

TEST APPLICABLE

For 47 CFR Part 15C section 15.247 (a) (1) requirement:

Frequency hopping systems shall have hopping channel carrier frequencies separated by a minimum of 25 kHz or the 20 dB bandwidth of the hop-ping channel, whichever is greater. Alternatively, frequency hopping systems operating in the 2400–2483.5 MHz band may have hopping channel carrier frequencies that are separated by 25 kHz or two-thirds of the 20 dB bandwidth of the hopping channel, whichever is greater, provided the systems operate with an output power no greater than 125 mW. The system shall hop to channel frequencies that are selected at the system hopping rate from a pseudo randomly ordered list of hopping frequencies. Each frequency must be used equally on the average by each transmitter. The system receivers shall have input bandwidths that match the hop-ping channel bandwidths of their corresponding transmitters and shall shift frequencies in synchronization with the transmitted signals.

EUT Pseudorandom Frequency Hopping Sequence Requirement

The pseudorandom frequency hopping sequence may be generated in a nice-stage shift register whose 5th and 9th stage outputs are added in a modulo-two addition stage. And the result is fed back to the input of the firststage. The sequence begins with the first one of 9 consecutive ones, forexample: the shift register is initialized with nine ones.

- Number of shift register stages:9
- Length of pseudo-random sequence:29-1=511 bits
- Longest sequence of zeros:8(non-inverted signal)

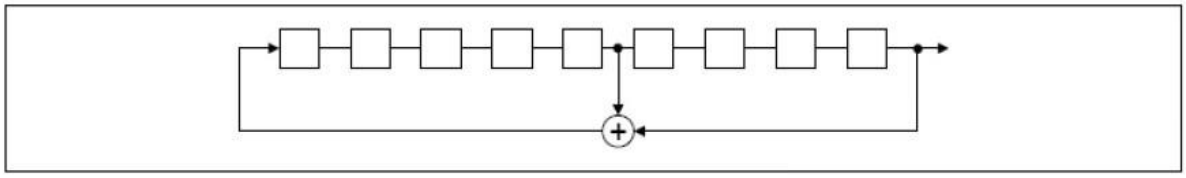

Linear Feedback Shift Register for Generation of the PRBS sequence

An example of pseudorandom frequency hopping sequence as follows:

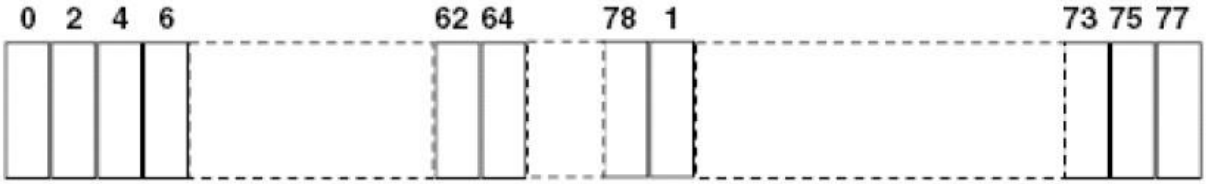

Each frequency used equally one the average by each transmitter.

The system receiver have input bandwidths that match the hopping channel bandwidths of their corresponding transmitter and shift frequencies in synchronization with the transmitted signals.

4.10 Antenna Requirement

Standard Applicable

For intentional device, according to FCC 47 CFR Section 15.203, an intentional radiator shall be designed to ensure that no antenna other than that furnished by the responsible party shall be used with the device.

And according to FCC 47 CFR Section 15.247 (c), if transmitting antennas of directional gain greater than 6dBi are used, the power shall be reduced by the amount in dB that the directional gain of the antenna exceeds 6dBi.

Refer to statement below for compliance

The manufacturer may design the unit so that the user can replace a broken antenna, but the use of a standard antenna jack or electrical connector is prohibited. Further, this requirement does not apply to intentional radiators that must be professionally installed.

Antenna Connected Construction

The maximum gain of antenna was 0dBi.

5 Test Setup Photos of the EUT

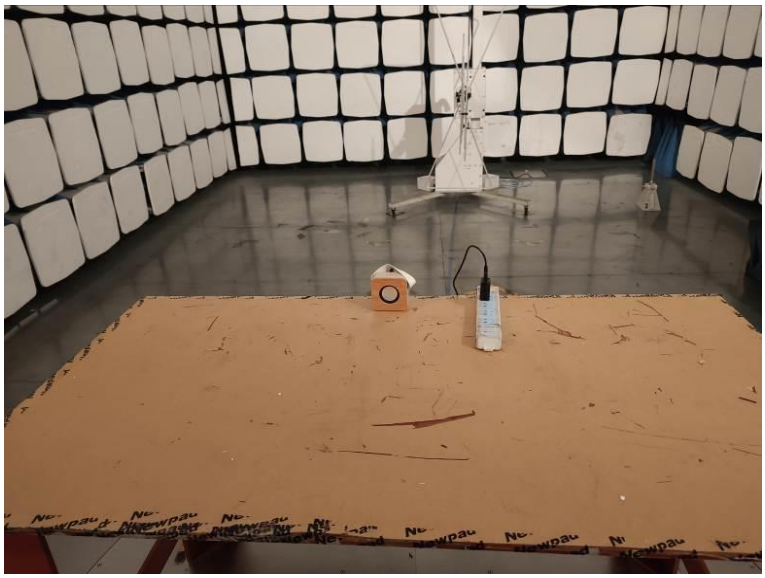

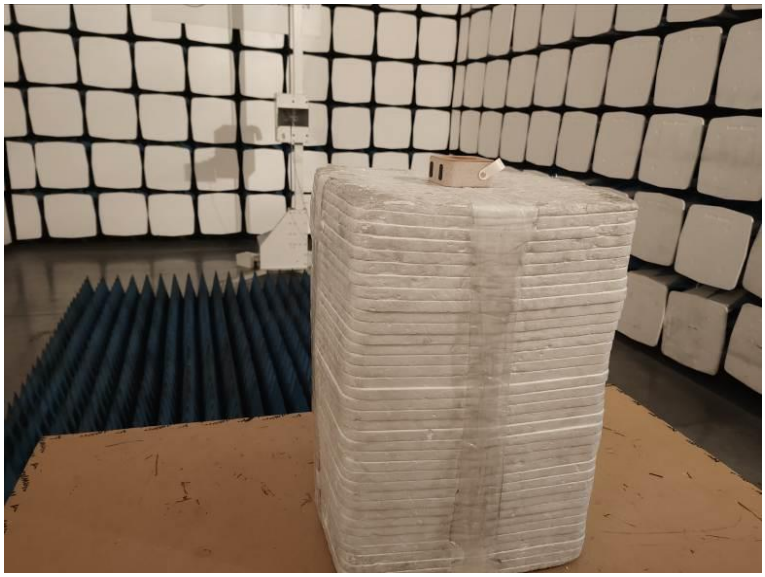

6 Photos of the EUT

External Photos of EUT

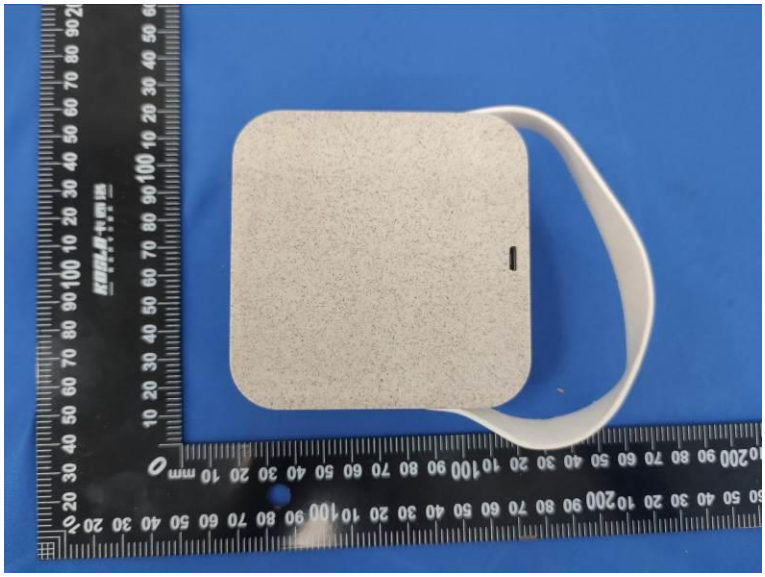

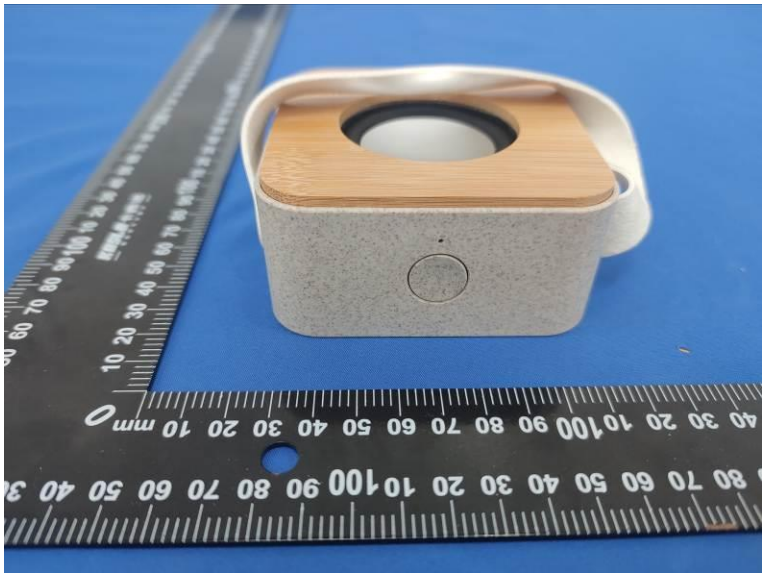

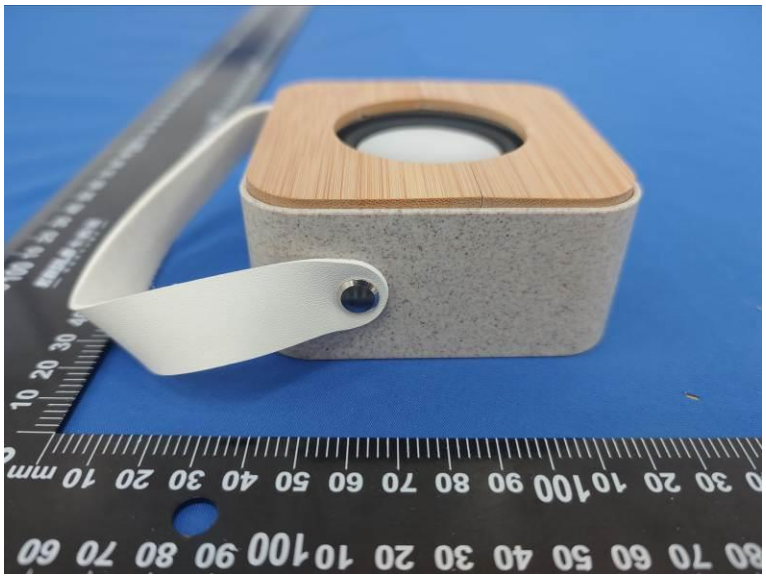

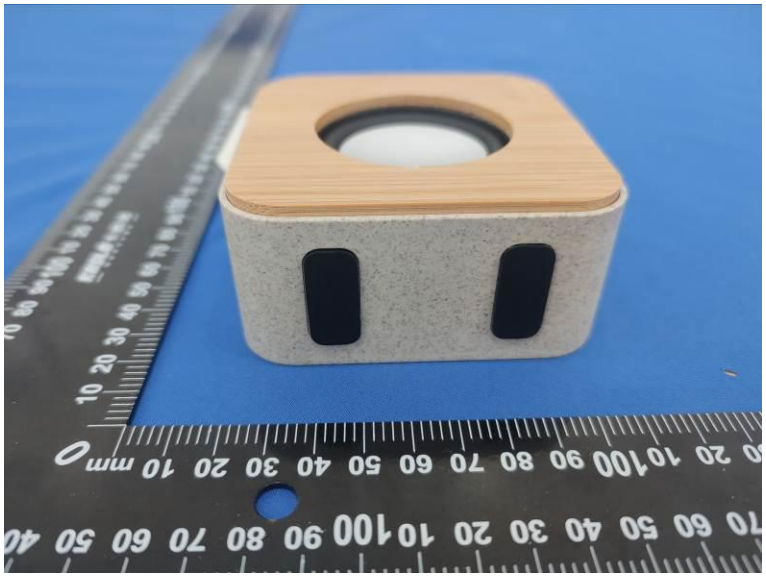

Internal Photos of EUT

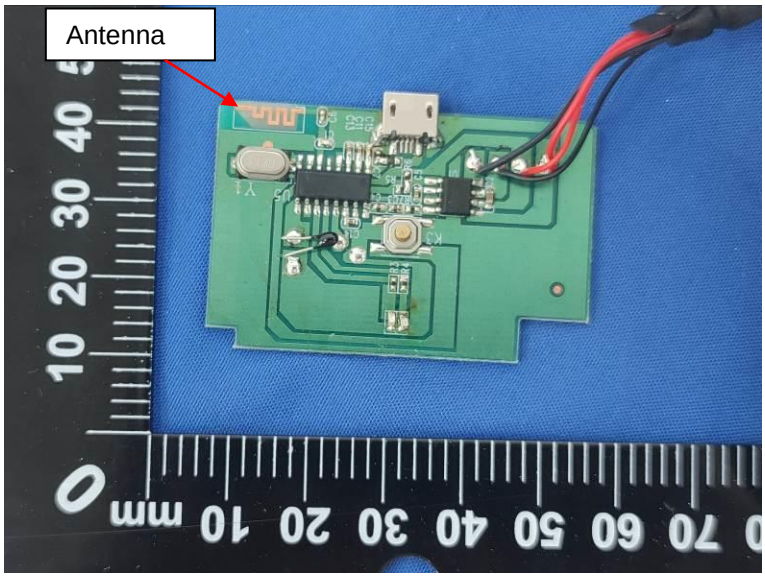

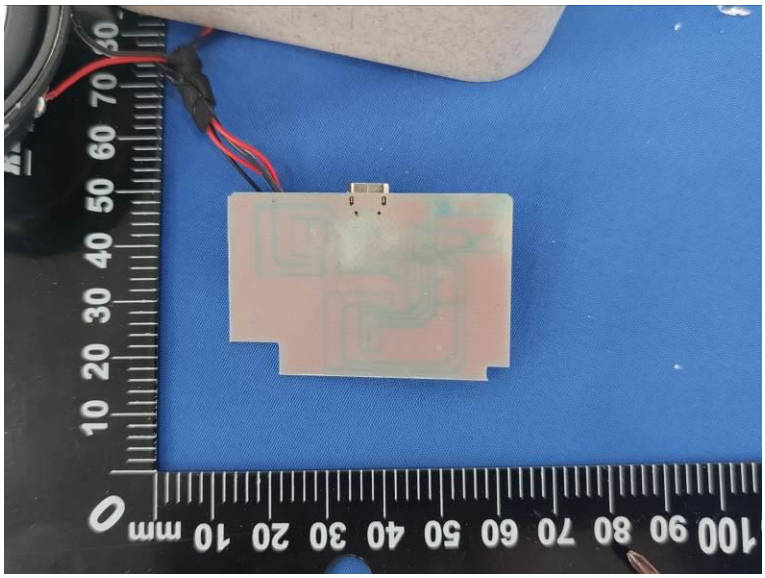

********** End of Report **********